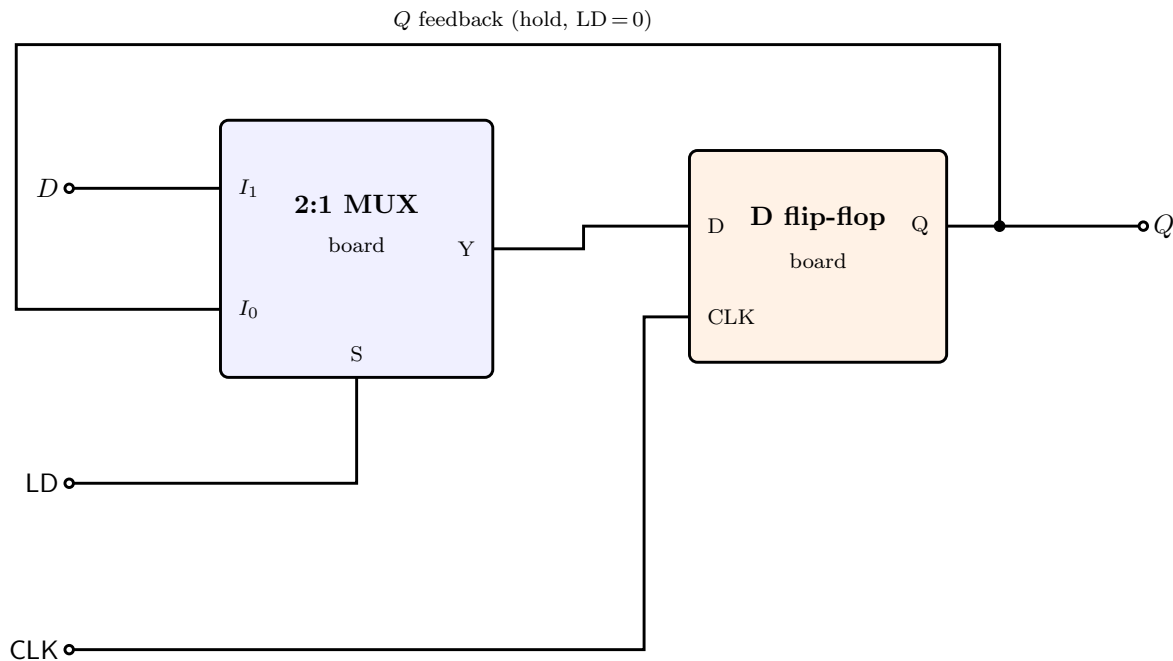




*The **2:1 MUX board** (see [mux-2-to-1](#)) picks D when $LD = 1$ or the fed-back Q when $LD = 0$, and hands it to the flip-flop. (Power pins left out: both boards also connect to $+5\text{ V}$ and GND .)*